

# Alternating Current Circuits




Time domain form

$\Delta V_{max}$   
amplitude

$$\Delta v = \Delta V_{max} \sin(\omega t - \phi)$$

↓  
amplitude
↓  
frequency
↓  
phase

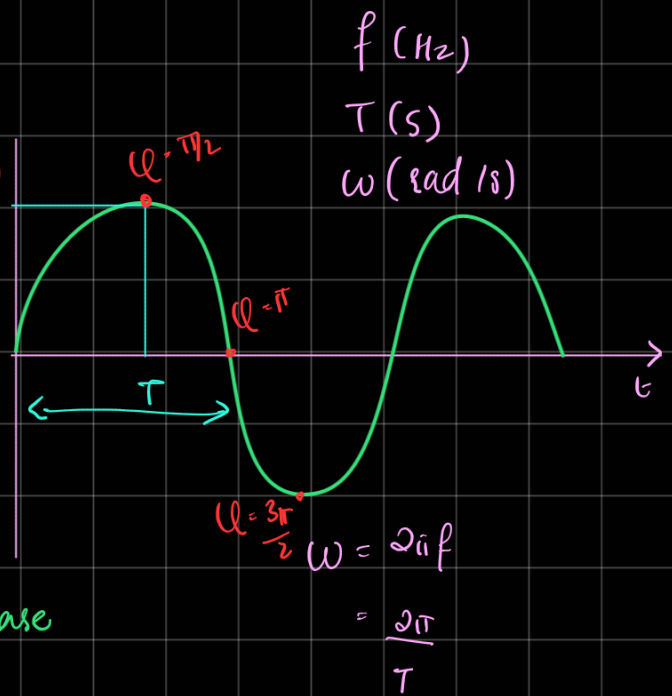


## Phasors

Length = Amplitude

Angle = Phase


Speed of rotation =  $\omega$

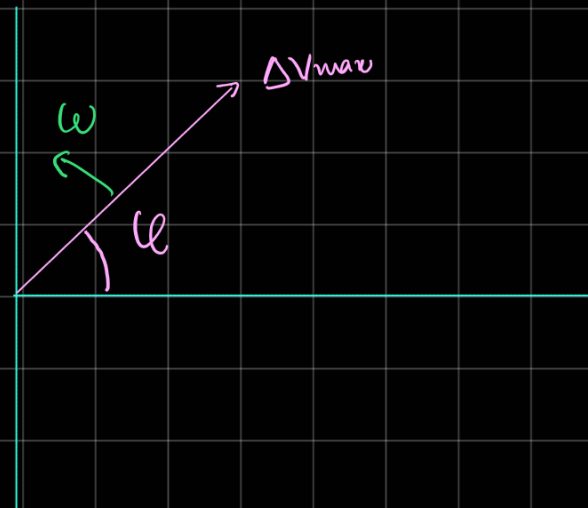

$$i_R = \frac{\Delta v}{R} = \frac{\Delta V_{max}}{R} \sin(\omega t)$$

$$= I_{max} \sin(\omega t)$$
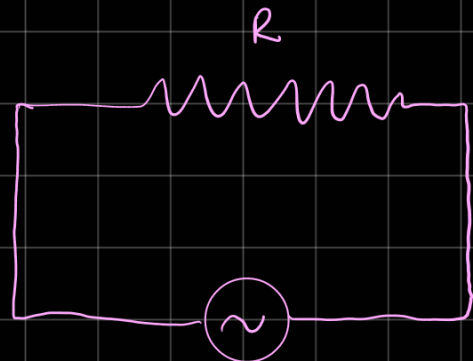
$$\Delta v_R = i_R R = I_{max} R \sin(\omega t)$$



$$\Delta v = \Delta V_{max} \sin(\omega t)$$

Current & voltage for a resistor are always in phase

$$P_{avg} = I_{rms}^2 R$$


↓  
root mean square

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$\Delta V_{rms} = \frac{\Delta V_{max}}{\sqrt{2}}$$



=

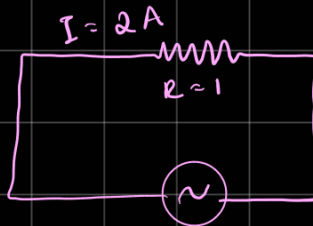

$$I = 1.414 \text{ A} = 2/\sqrt{2}$$


$$\Delta V_{max} = 2 \text{ V}$$

$$\Delta V_L = \Delta V_{max} \sin(\omega t)$$

$$i_L = \frac{\Delta V_{max}}{X_L} \sin(\omega t - \pi/2)$$

$$\phi = 0$$

$$\phi = -\pi/2$$

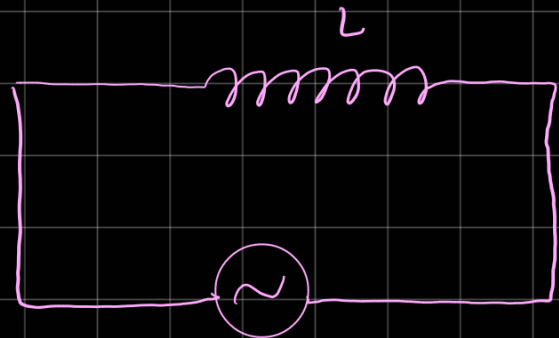

$$\Delta V_L = \Delta V_{max} \sin(\omega t)$$

The current 'lags' behind the voltage by  $\pi/2$

$$X_L = \omega L = 2\pi f L \Rightarrow \text{inductive reactance } (\Omega)$$

$$f \uparrow$$

$$X_L \uparrow$$

$L \rightarrow$  open circuit


$$f \downarrow$$

$$X_L \downarrow$$

$L \rightarrow$  short circuit

$$\Delta V_C = \Delta V_{max} \sin(\omega t)$$
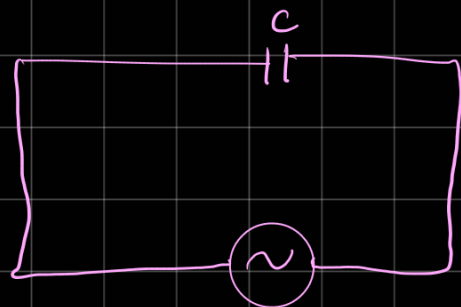
$$i_C = \frac{\Delta V_{max}}{X_C} \sin(\omega t + \pi/2)$$



The current 'leads' the voltage by  $\pi/2$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$f \uparrow$   
 $X_C \downarrow$

$C \rightarrow$  short circuit

$f \downarrow$   
 $X_C \uparrow$

$C \rightarrow$  open circuit

$$i = \frac{\Delta v}{Z} = \frac{\Delta V_{\max} \sin(\omega t - \phi)}{Z}$$

$$i = I_{\max} \sin(\omega t - \phi)$$

$Z \Rightarrow$  impedance ( $\Omega$ )

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$\phi$  phase angle (degree)  $\tan^{-1} \left[ \frac{X_L - X_C}{R} \right]$

$X_L = X_C \Rightarrow i$  &  $\Delta v$  are in phase

$$Z = \sqrt{R^2 + 0^2} = R$$

Circuit is purely resistive

$$\phi = 0$$

$X_L > X_C \Rightarrow$  more inductive than capacitive


$\phi$  is positive

current lags behind voltage

$X_L < X_C \Rightarrow$  more capacitive than inductive

$\phi$  is negative

current leads the voltage

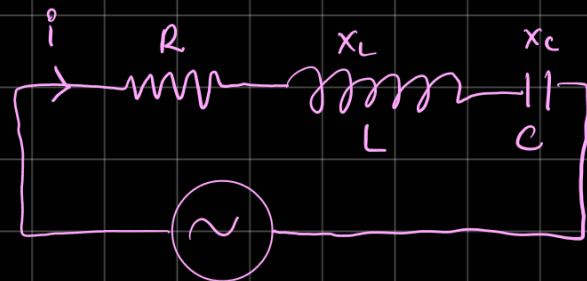

$$\Delta v = \Delta V_{\max} \sin(\omega t)$$

$$X_L = X_C \Rightarrow \omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

resonance  
resonant frequency  
maximum current

In RLC circuit

$$P_{avg} = \frac{1}{2} I_{max} V_{max} \cos \phi$$

$$= I_{rms} V_{rms} \cos \phi$$

$$= I_{rms}^2 R$$

$\cos \phi \Rightarrow$  power factor

Power as function of frequency

$$Q = \frac{\omega_0}{\Delta \omega} = \frac{\omega_0 L}{R}$$

half power point

