

$$I = \frac{\Delta V}{R}$$

\mathcal{E} : Electromagnetic Force (EMF)
Voltage written on batteries


$$I = \frac{\mathcal{E}}{R + r}$$

$$P_{\text{batt}} = I\mathcal{E} = I^2 r + I^2 R$$

$$R = \frac{\Delta V^2}{P} = \frac{(11.6)^2}{20} = 6.728$$

$$I = \frac{\Delta V}{R} = \frac{11.6}{6.7} = 1.72 \text{ A}$$
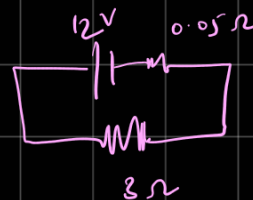
$$r = \frac{\Delta V}{I} = 1.972 \Omega$$



$$a) I = \frac{\mathcal{E}}{R + r} = \frac{12}{3 + 0.05} = 3.93 \text{ A}$$

$$\Delta V_R = \mathcal{E} - I r = 11.8035 \text{ V}$$


$$\Delta V_r = 0.1965 \text{ V}$$

$$b) P_r = I^2 r = 0.77 \text{ W}$$

$$P_R = I^2 R = 46.33 \text{ W}$$

$$P = I\mathcal{E} = 47.16 \text{ W}$$

Resistors in series

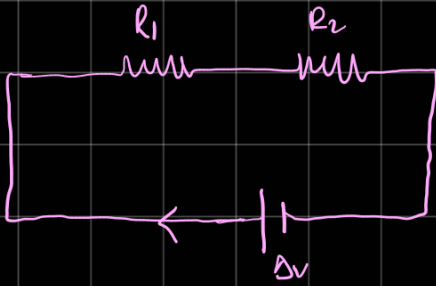

$$R_{eq} = R_1 + R_2$$

$$I = I_1 = I_2$$

$$\Delta V = \Delta V_1 + \Delta V_2$$

$$\Delta V_1 = I \cdot R_1 \quad \Delta V_2 = I \cdot R_2$$

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{3} + \frac{1}{6} + \frac{1}{9} \\ &= \frac{6}{18} + \frac{3}{18} + \frac{2}{18} \\ &= \frac{11}{18} \end{aligned}$$

$$R_{eq} = \frac{18}{11}$$

$$I_1 = \frac{\Delta V}{R_1} = \frac{18}{3} = \underline{6 \text{ A}}$$

$$I_2 = \frac{\Delta V}{R_2} = \frac{18}{6} = \underline{3 \text{ A}}$$

$$I_3 = \frac{\Delta V}{R_3} = \frac{18}{9} = \underline{2 \text{ A}}$$

$$I = I_1 + I_2 + I_3 = 11 \text{ A}$$

Resistors in parallel



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I = I_1 + I_2$$

$$\Delta V = \Delta V_1 = \Delta V_2$$

$$I_1 = \frac{\Delta V_1}{R_1} \quad I_2 = \frac{\Delta V_2}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{2}{R}$$

$$R_{eq} = \frac{R}{2}$$

$$R_{eq} = \frac{R}{3} + 2R = \frac{7R}{3} \Omega$$

Kirchoff's Law

KVL

Kirchoff's
Voltage
Law



Define direction
of the loop

KCL

Kirchoff's
Current-
Law



Sum of currents entering a junction
= Sum of currents leaving a junction

Exam Question

KCL

Assume any direction of current

Write KCL $I_1 + I_2 = I_3$

KVL

Define loops

If battery terminal +ve, then write -ve

$$I_1 + I_2 = I_3$$

$$-14 + 6I_1 - 10 - 4I_2 = 0$$

$$-2I_1 + 12I_2 - 6I_3 = 0$$

$$2I_3 + 10 - 6I_1 = 0$$

$$6I_1 - 4I_2 = 24$$

$$-2I_1 - 2I_2 + 10 - 6I_1 = 0$$

$$-8I_1 - 2I_2 = -10$$

$$8I_1 + 2I_2 = 10$$

$$6I_1 - 4I_2 = 24 \quad \text{--- (i)}$$

$$8I_1 + 2I_2 = 10 \quad \text{--- (ii)}$$

$$\text{(i)} + 2\text{(ii)}$$

$$(6+16)I_1 = 44$$

$$22I_1 = 44$$

$$I_1 = \underline{2 \text{ A}}$$

$$6(2) - 4I_2 = 24$$

$$-4I_2 = 24 - 12$$

$$I_2 = \underline{\underline{-\frac{12}{4}}}$$

$$= \underline{\underline{-3 \text{ A}}}$$

$$I_3 = I_1 + I_2$$


$$= 2 + 3$$

$$= \underline{\underline{-1 \text{ A}}}$$

$$I_1 = I_2 + I_3$$

$$6I_3 - 8 + 2I_1 = 0$$


$$\rightarrow -2I_1 - 12 - 4I_2 = 0$$

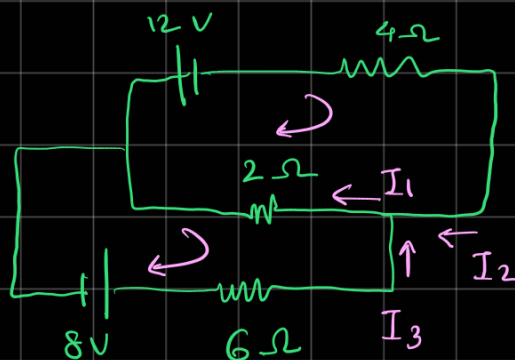

$$6I_3 - 8 + 2I_2 + 2I_3 = 0$$

$$2I_2 + 8I_3 = 8$$

$$3I_2 + I_3 = 6$$

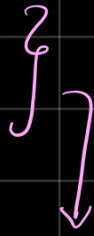

$$6I_2 + 24I_3 = 24$$

$$6I_2 + 2I_3 = 12$$



$$22I_3 = 12$$

$$I_3 = \frac{12}{22} = \frac{6}{11}$$

$$6I_2 = 12 - \frac{12}{11}$$

$$I_2 = \frac{11 \times 12 - 12}{66}$$

$$= \frac{12(11 - 1)}{66}$$

$$= \frac{6 \times 20}{6 \times 11}$$

$$= \frac{20}{11}$$

$$I_1 = \frac{20}{11} + \frac{6}{11} = \frac{26}{11}$$

$$2I_1 + 4I_2 = 12$$

$$6I_2 + 2I_3 = 12$$

$$3I_2 + I_3 = 6$$

RC Circuits

$$C = \frac{Q}{\Delta V} \Rightarrow Q_{\max} = CE$$

when capacitor reaches voltage of battery, charge drops to zero
fully charged

Charging

$$q(t) = \underbrace{Q_{\max}}_{CE} (1 - e^{-t/\tau})$$

Time constant
time taken to reach 63% of Q_{\max}

$$\tau = RC$$

$$i(t) = \underbrace{\frac{\mathcal{E}}{R}}_{I_{\max}} e^{-t/\tau}$$

Discharging

$$q(t) = Q_i e^{-t/\tau} \qquad i(t) = \frac{Q_i}{RC} e^{-t/\tau}$$

Time taken to reach 36% of initial charge

$$\tau = 20 \times 100 = 2000 \mu s$$
$$= 2 \text{ ms}$$

$$Q_{\max} = CE$$
$$= 20 \mu F \times 9 \text{ V}$$
$$= 180 \mu C$$

$$q(\tau) = 0.63 \times 180 \mu C$$
$$= 113.4 \mu C$$

