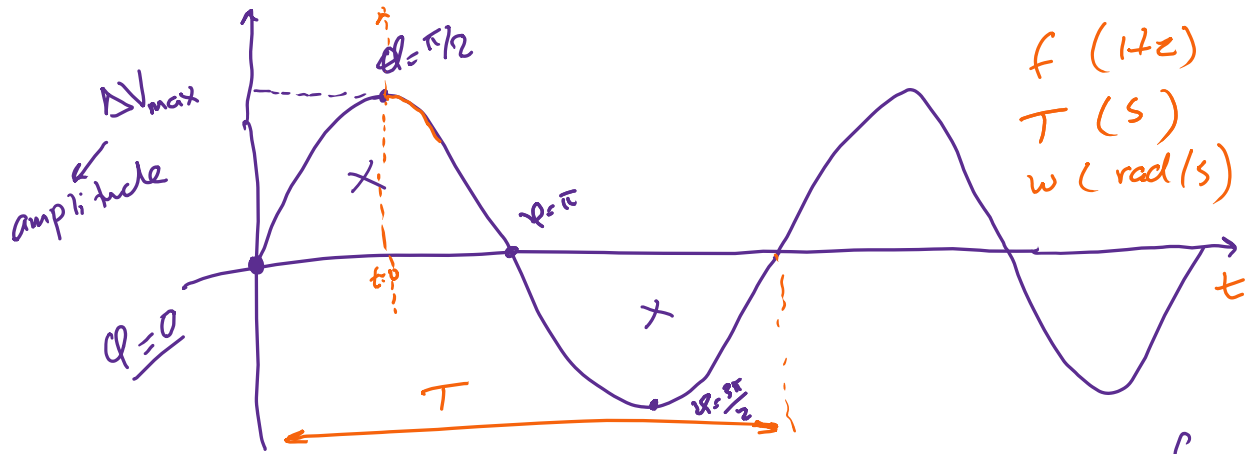


periodic



time-domain

$$\Delta V = \Delta V_{\max} \sin(\omega t + \phi)$$

amplitude


$$\sin(\omega t + \phi)$$

frequency

phase

$$\omega = 2\pi f = \frac{2\pi}{T}$$


Phasors:

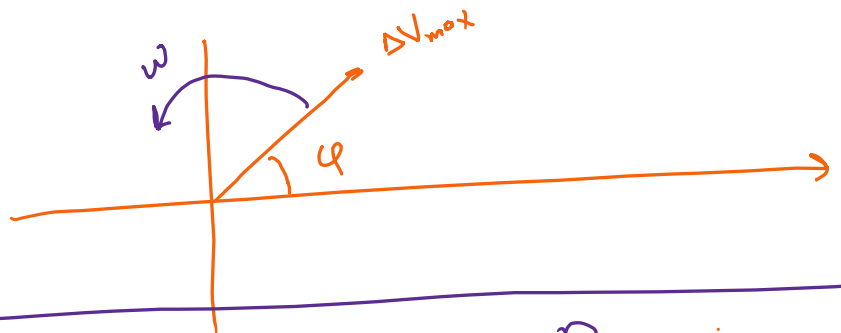

$$i_R = \frac{\Delta V}{R} = \frac{\Delta V_{\max}}{R} \sin(\omega t)$$

$$i_R = I_{\max} \sin(\omega t) \quad \phi = 0$$
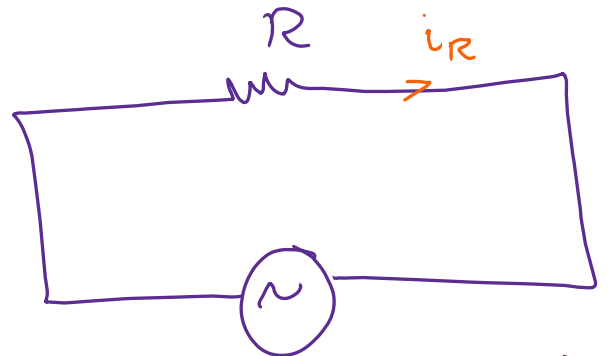
$$\Delta V_R = i_R R = I_{\max} R \sin(\omega t) \quad \phi = 0$$



$$\Delta V = \Delta V_{\max} \sin(\omega t)$$


alternating value

constant value

Current & voltage for a resistor are always in phase!


$$P = I_{\text{rms}}^2 R$$

root mean square

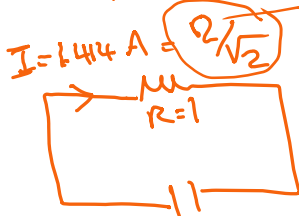

$$I_{\text{rms}} = \frac{I_{\max}}{\sqrt{2}}$$


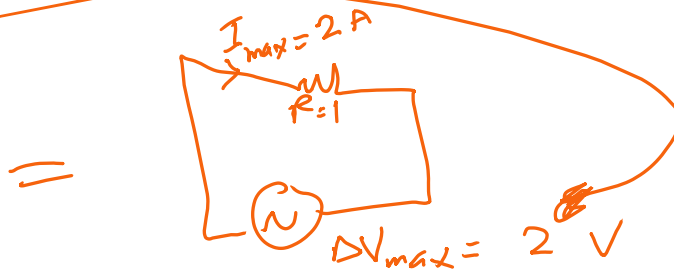
$$\Delta V_{\text{rms}} = \frac{\Delta V_{\max}}{\sqrt{2}}$$



$$\Delta V_L = \Delta V_{\max} \sin(\omega t)$$

$$i_L = \frac{\Delta V_{\max}}{X_L} \sin(\omega t - \frac{\pi}{2})$$

I_{\max} ←

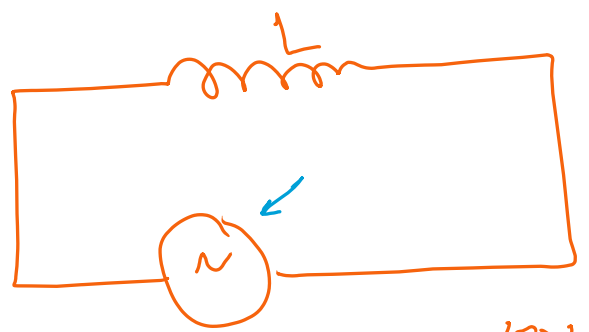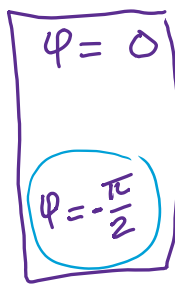

Current always lags the voltage by $\frac{\pi}{2}$ $\Delta V = \Delta V_{\max} \sin(\omega t)$

$$X_L = \omega L = 2\pi f L \Rightarrow \text{inductive Reactance } (\Omega)$$

$f \uparrow$
 $X_L \uparrow$
 $L \rightarrow$ open circuit

$f \downarrow$
 $X_L \downarrow$
 $L \rightarrow$ short circuit

$$\text{DC} \rightarrow f = 0$$


$$X_L = 0$$

$$\Delta V_C = \Delta V_{\max} \sin(\omega t)$$

$$\phi = 0$$

$$i_C = \frac{\Delta V_{\max}}{X_C} \sin(\omega t + \frac{\pi}{2})$$

$\phi = \frac{\pi}{2}$

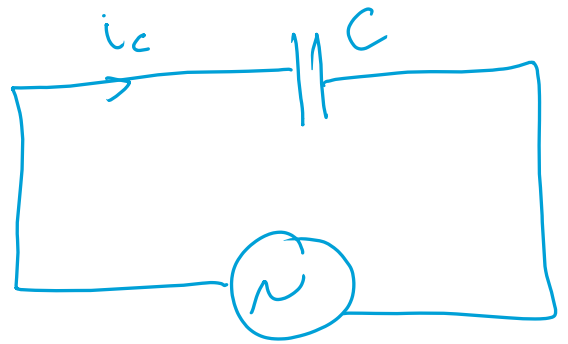

current always leads the voltage by $\frac{\pi}{2}$ $\Delta V = \Delta V_{\max} \sin(\omega t)$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} (\Omega)$$

$f \uparrow$
 $X_C \downarrow$
 short circuit


$f \downarrow$
 $X_C \uparrow$
 open circuit

$$\text{DC} \rightarrow f = 0$$

$$X_C = \infty$$

$$i = \frac{\Delta v}{Z} = \frac{\Delta v_{\max} \sin(\omega t - \varphi)}{Z}$$
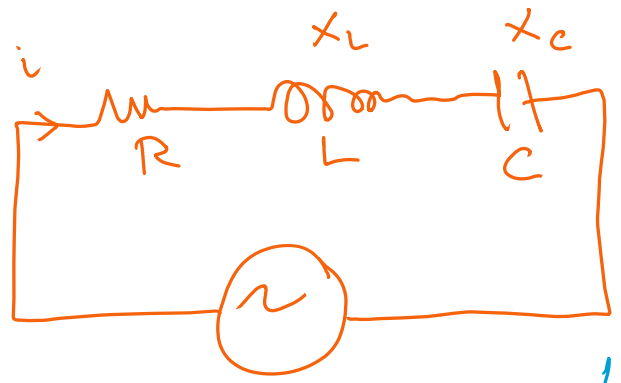
$$i = I_{\max} \sin(\omega t - \varphi)$$



$$\Delta v = \Delta v_{\max} \sin(\omega t)$$

$Z \Rightarrow$ impedance (Ω)

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

φ : phase angle (degree) =

$$\tan^{-1} \left[\frac{X_L - X_C}{R} \right]$$

$X_L = X_C \Rightarrow i$ & Δv in phase

$$\Rightarrow Z = \sqrt{R^2 + 0^2} = R \Rightarrow \text{purely resistive}$$

$$\Rightarrow \varphi = 0$$

$$X_L > X_C$$

\Rightarrow more inductive than capacitive

$\Rightarrow \varphi$ is positive

\Rightarrow current lags the voltage

$$X_L < X_C$$

\Rightarrow more capacitive than inductive

$\Rightarrow \varphi$ is negative

\Rightarrow current leads the voltage

$$X_L = X_C \Rightarrow \omega L = \frac{1}{\omega C} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

resonance

The maximum current in the circuit \leftarrow resonant frequency

$$\begin{aligned}\text{In RLC} \Rightarrow P_{av} &= \frac{1}{2} I_{\max} V_{\max} \cos \varphi \\ &= I_{\text{rms}} V_{\text{rms}} \cos \varphi \\ &= \overset{-2}{I}_{\text{rms}} R \checkmark\end{aligned}$$

$\cos \varphi \Rightarrow$ power factor