

PHYS143

Physics for Engineers

Tutorial - Chapter 33

Question 1

The output voltage of an AC source is given by $\Delta v = 120 \sin 30.0\pi t$, where Δv is in volts and t is in seconds. The source is connected across a 0.500-H inductor. Find (a) the frequency of the source, (b) the rms voltage across the inductor, (c) the inductive reactance of the circuit, (d) the rms current in the inductor, and (e) the maximum current in the inductor.

Question 2

A source delivers an AC voltage of the form $\Delta v = 98.0 \sin 80\pi t$, where Δv is in volts and t is in seconds, to a capacitor. The maximum current in the circuit is 0.500 A. Find (a) the rms voltage of the source, (b) the frequency of the source, and (c) the value of the capacitance.

Question 3

An AC voltage of the form $\Delta v = 90.0 \sin 350t$, where Δv is in volts and t is in seconds, is applied to a series RLC circuit. If $R = 50.0 \, \Omega$, $C = 25.0 \, \mu\text{F}$, and $L = 0.200 \, \text{H}$, find (a) the impedance of the circuit, (b) the rms current in the circuit, and (c) the average power delivered to the circuit.

Question 4

A series RLC circuit has components with the following values: $L = 20.0 \, \text{mH}$, $C = 100 \, \text{nF}$, $R = 20.0 \, \Omega$, and $\Delta V_{\text{max}} = 100 \, \text{V}$, with $\Delta v = \Delta V_{\text{max}} \sin \omega t$. Find (a) the resonant frequency of the circuit, (b) the amplitude of the current at the resonant frequency, (c) the Q of the circuit, and (d) the amplitude of the voltage across the inductor at resonance.

Question 5

A step-down transformer is used for recharging the batteries of portable electronic devices. The turns ratio N_2/N_1 for a particular transformer used in a DVD player is 1:13. When used with 120-V (rms) household service, the transformer draws an rms current of 20.0 mA from the house outlet. Find (a) the rms output voltage of the transformer and (b) the power delivered to the DVD player.

Question 6

The RC high-pass filter shown in Figure has a resistance $R = 0.500 \, \Omega$ and a capacitance $C = 613 \, \mu\text{F}$. What is the ratio of the amplitude of the output voltage to that of the input voltage for this filter for a source frequency of 600 Hz?

