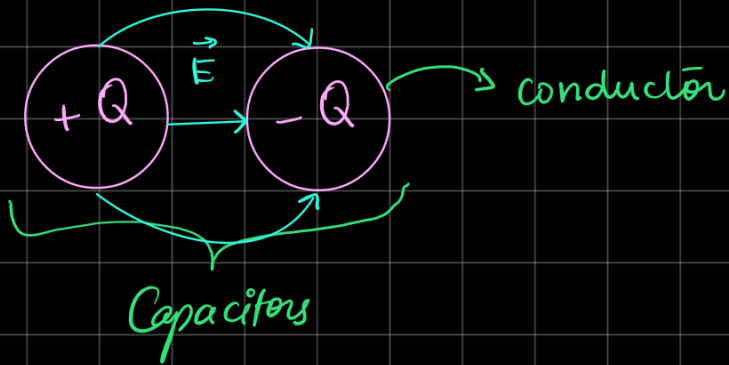


# Capacitance & Dielectrics



$$C = \frac{Q}{\Delta V}$$

Charge of conductors

Voltage created by electric field

Capacitance

always +ve


always constant, regardless of charge on conductor

$$\Delta V = \vec{E} \cdot \vec{d}$$

applies for all capacitor types

$$\text{Unit} \Rightarrow \text{Farad (F)} = \frac{\text{Coulomb}}{\text{Volt}}$$

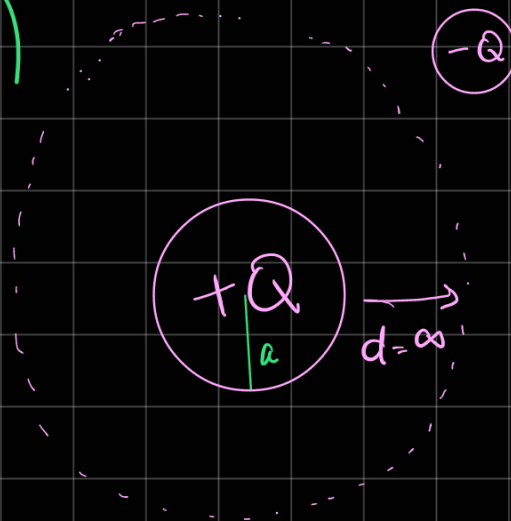Isolated Sphere  
(-ve charge at infinity)



$$C = 4\pi\epsilon_0 a$$

$$Q$$

$$a$$

capacitance of

$$C = \frac{Q}{\Delta V} = \frac{Q}{k_e Q/a} = \frac{a}{k_e}$$

isolated sphere

$\hookrightarrow 8.85 \times 10^9$

Parallel  
Plates

$$C = \frac{Q}{\Delta V} = \frac{Q}{\vec{E} \cdot \vec{d}}$$

$$= \frac{Q}{\frac{\sigma}{\epsilon_0} d}$$


$$= \frac{Q}{\frac{Q}{A} \cdot \frac{1}{\epsilon_0} d}$$

$$= \frac{A \epsilon_0}{d}$$





Permittivity of space  $8.5 \times 10^{-12}$

$\hookrightarrow$  distance b/w plates

$\nwarrow$  area of plate

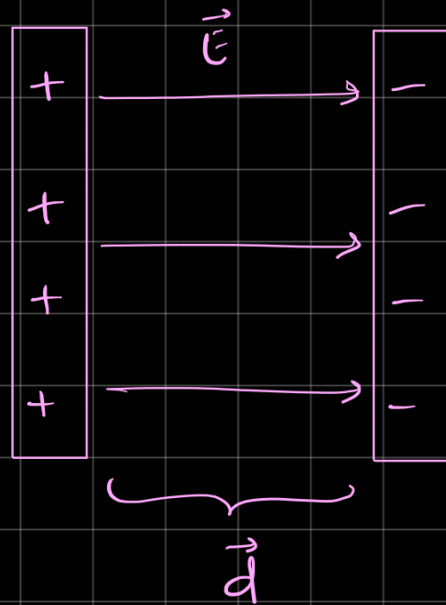

## Electric Symbols

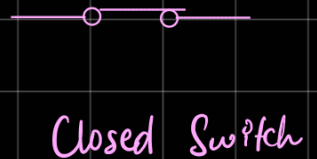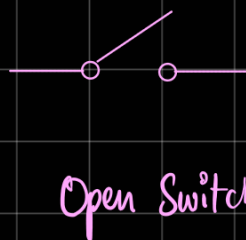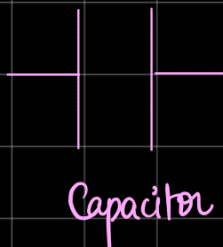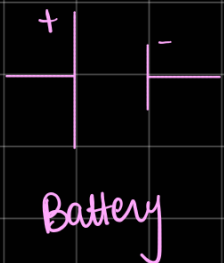

## Capacitors in Parallel

$$Q_1 C_1 10 \mu F$$




$$Q_{eq}$$

$$\Delta V$$

$$C_{eq} = 40 \mu F$$



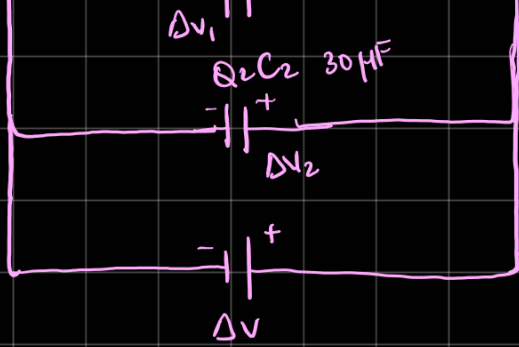

$$C_{eq} > C_1, C_2$$


$$C_{eq} = C_1 + C_2$$

$$\Delta V_1 = \Delta V_2$$

$$Q_{eq} = Q_1 + Q_2$$



## Capacitors in Series

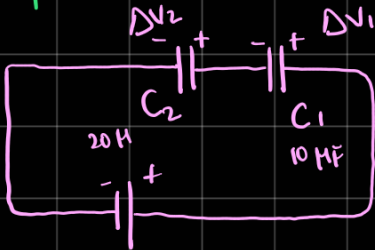


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{10}$$

$$= \frac{3}{20}$$

$$C_{eq} < C_1, C_2$$

$$C_{eq} = \frac{20}{3} \mu F$$

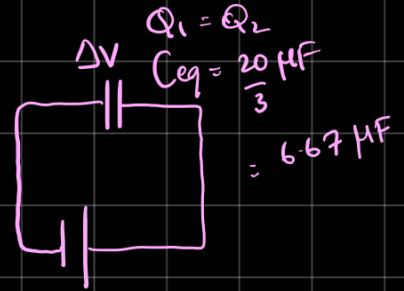

$$Q_1 = Q_2$$

$$C_{eq} = \frac{20}{3} \mu F$$

$$= 6.67 \mu F$$

$$\Delta V = \Delta V_1 + \Delta V_2$$

$$Q_1 = Q_2$$

## Example

$$C_{eq1} = 4 \mu F$$

$$C_{eq2} = \frac{1}{4} + \frac{1}{4} = 2 \mu F$$

$$C_{eq3} = 8 \mu F$$

$$C_{eq4} = \frac{1}{8} + \frac{1}{8} = 4 \mu F$$

$$C_{eq} = 4 + 2 = 6 \mu F$$

### Example

a)  $C_{eq} = 17 \mu F$

b)  $\Delta V = 9 V$

c)  $Q_1 = C_1 \cdot \Delta V$

$$= 5 \times 9$$

$$= 45 \mu C$$

$$Q_2 = C_2 \Delta V$$

$$= 12 \times 9$$


$$= 108 \mu C$$

### Example

$$C_1 = 5 \mu F$$


$$C_2 = 10 \mu F$$

$$C_3 = 2 \mu F$$

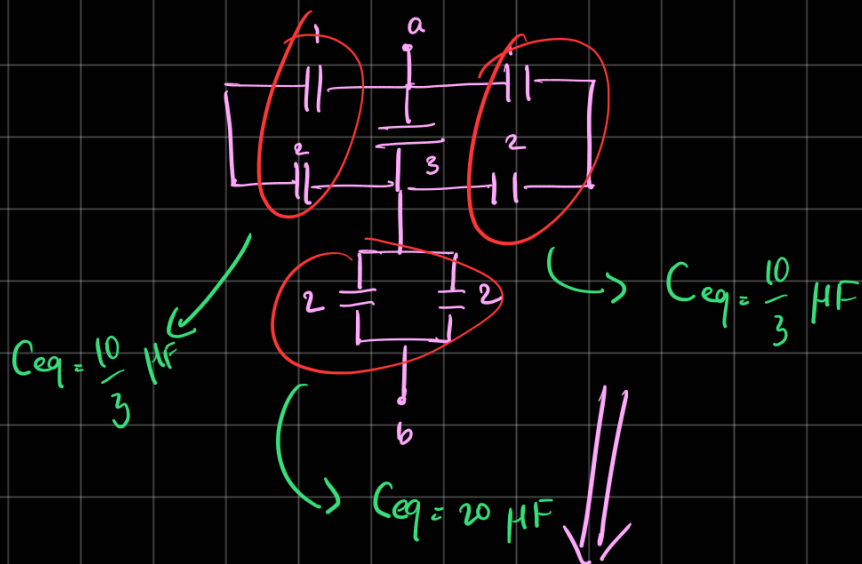

$$\frac{10}{3} + \frac{10}{3} + 2$$

$$= \frac{26}{3}$$

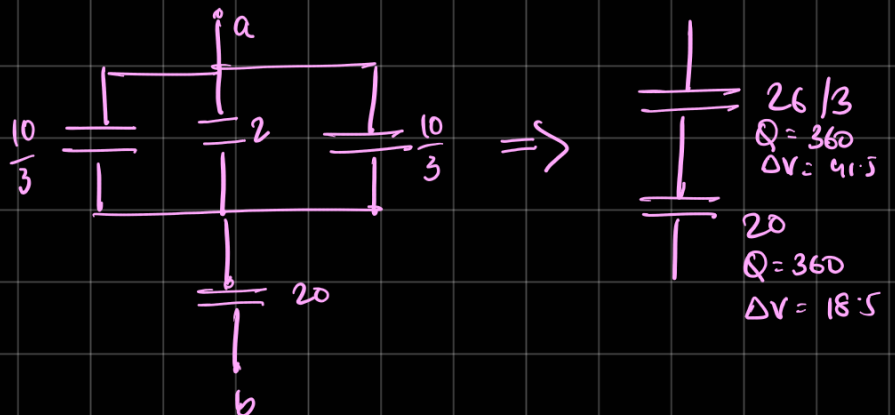

$$\frac{1}{C_{eq}} = \frac{3}{26} + \frac{1}{20}$$

$$= \frac{60 + 26}{20 \times 26}$$

$$= 86$$

$$= \frac{20 \times 26}{81}$$

$$= 6.05 \mu F$$

$$V = 60 V$$

$$C = \frac{Q}{\Delta V}$$

$$Q_{eq} = C \cdot \Delta V$$

$$= 6 \times 60$$

$$= 360 \mu C$$

$$Q_3 = C_3 \Delta V_3$$

$$= 2 \times 41.5$$

$$= 83 \mu C$$

Energy stored on capacitors

$$U_E = \frac{Q^2}{2C} = \frac{Q^2}{2 \frac{Q}{\Delta V}} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2$$

$$C = \frac{Q}{\Delta V}$$

$$Q = C \Delta V$$

Parallel plate

$$C = \frac{A \epsilon_0}{d}$$


$$U_E = \frac{Q^2}{2C} = \frac{d Q^2}{2 A \epsilon_0} = \frac{1}{2} \frac{A \epsilon_0}{d} (\vec{E} \cdot \vec{d})^2$$

$$= \frac{1}{2} A E^2 d \epsilon_0$$

Energy Density

$$\frac{U_E}{\text{Volume}} = \frac{\frac{1}{2} \epsilon_0 A d E^2}{A d}$$
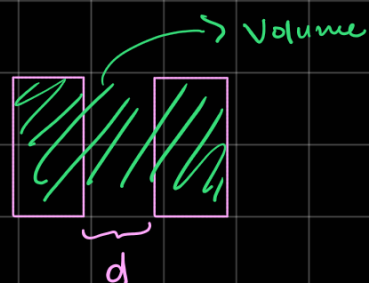
$$= \frac{1}{2} \epsilon_0 E^2 \text{ J/m}^3$$



## Dielectric


↳ insulator

inserted between +ve and negative plate

increases capacitance

makes capacitor more solid & rigid


$$C = \frac{k \epsilon_0 A}{d}$$

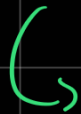

Dielectric constant

max. electric field

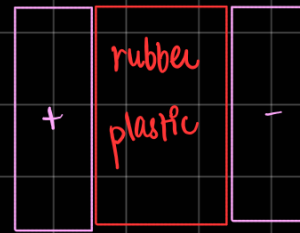that can be handled by  
insulator before it becomes  
a conductor



dielectric

## Dipole

dipole starts rotating in  
electric field  
generates torque

$$\vec{\tau} = \vec{P} \times \vec{E} = PE \sin \theta$$


↳ cross product

↳ Electric dipole moment

$$\vec{P} = 2aQ$$

$$U_E = -\vec{P} \cdot \vec{E} = -PE \cos \theta$$

↓  
dot product

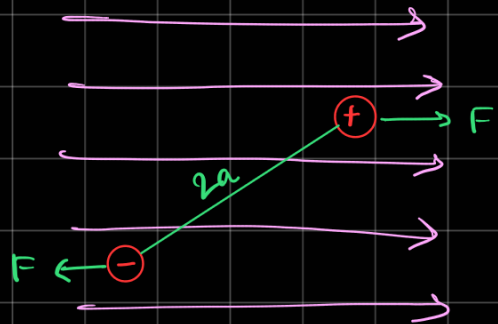

net  $F = 0$

## Example

$$U_E = \frac{Q^2}{2C}$$

$$= \frac{Q^2}{2Q/\Delta V}$$

$$= \frac{1}{2} Q \Delta V$$

$$= \frac{1}{2} \times 54 \times 12$$

$$= 324 \text{ J}$$

Example

$$U_C = \frac{Q^2}{2C}$$

b) parallel

Example

$$C \uparrow \quad Q \uparrow \quad \Delta V = \quad U_E \uparrow$$

Example

$$C = \frac{k \epsilon_0 A}{d}$$

$$= \frac{100 \times 8.85 \times 10^{-12} \times 1 \times 10^{-4}}{1 \times 10^{-3}}$$

$$8.85 \times 10^{-11} \text{ F}$$

Example

$$U_0 = \frac{Q^2}{2C} \longrightarrow \text{before}$$

$$U_0 = \frac{Q^2}{2kC} \longrightarrow \text{after}$$

